

PROJECT REPORT

MINI SIGNAL GENERATOR

Team Members :

IMT2020511 - Sirigiri Sai Keerthan

IMT2020513 - Vishal Cheeti

IMT2020533 – Dheeraj Sairam


IMT2020540 – Sasank Karamsetty

IMT2020541 – Vamsidhar Reddy


IMT2020555 – Ayyappa Koppuravuri

- We generated different signals using 555 timer chips
- We built a prototype which gives square, triangle, sine and cosine signals.
- We used potentiometers to adjust the amplitude of the signals.
- Later we used muxes to showcase our signals.


Sine Wave :

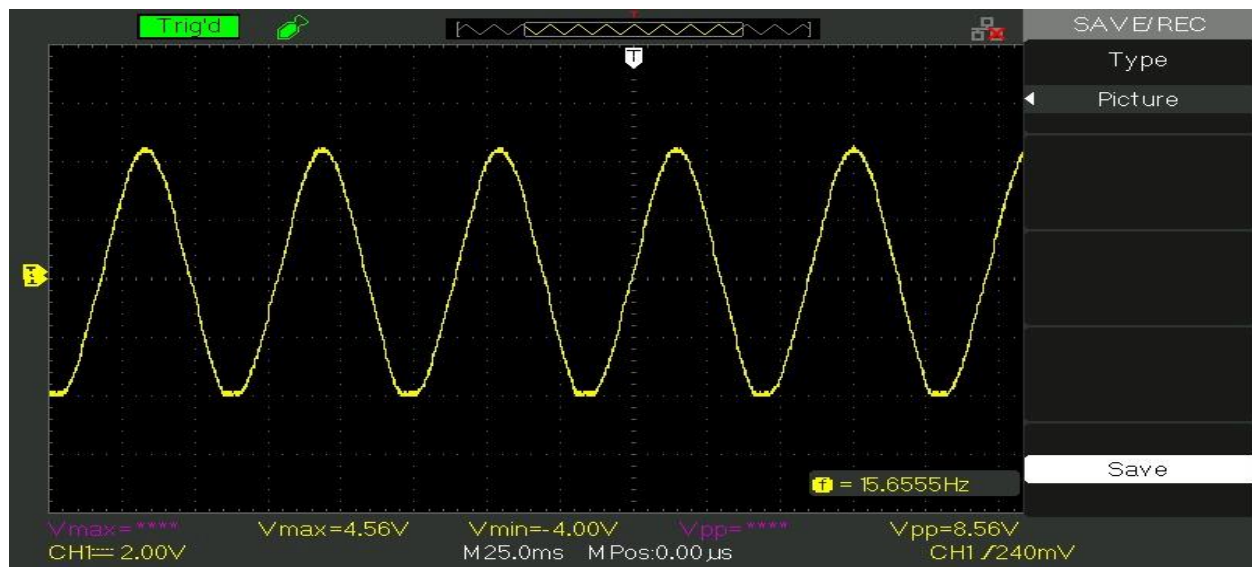


Triangle and Square Waves :

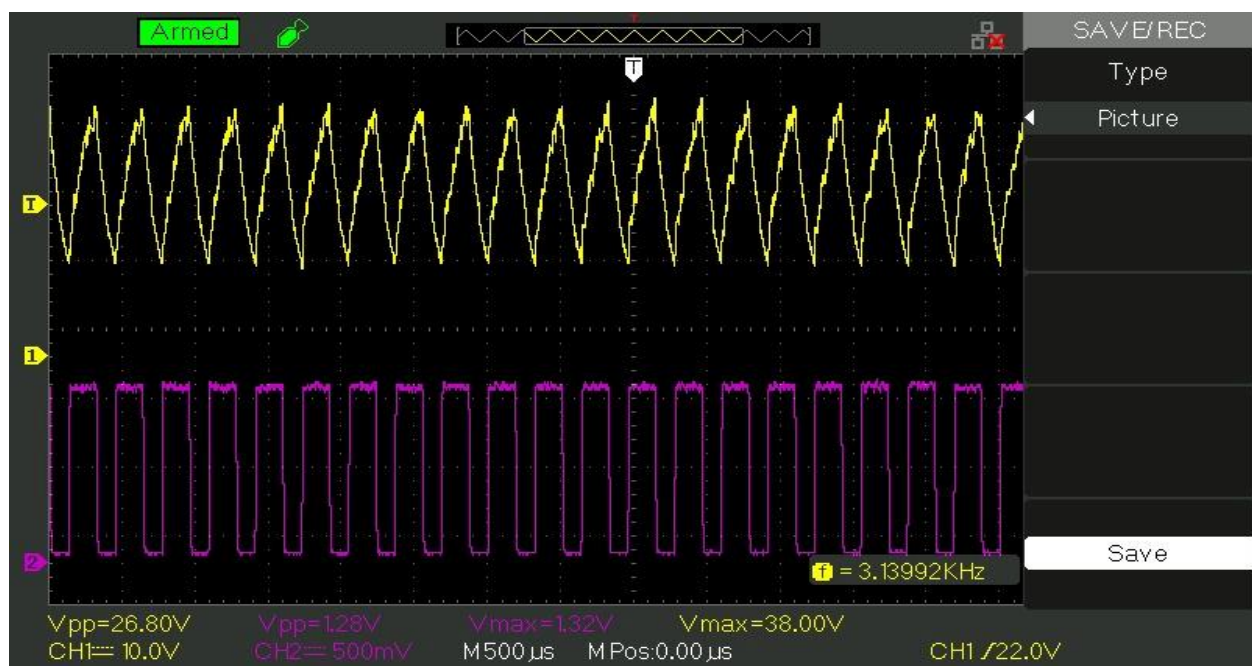


Sine and Cosine waves :

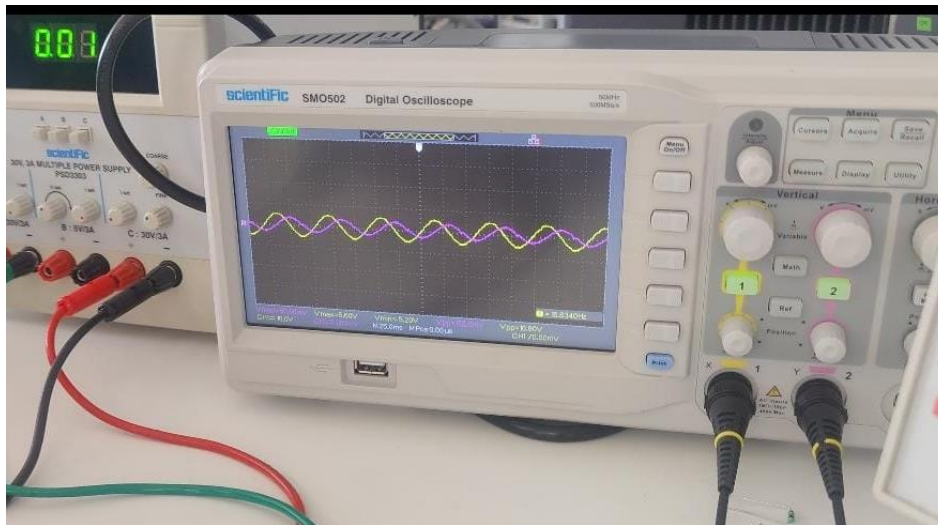


Triangle and square waves :

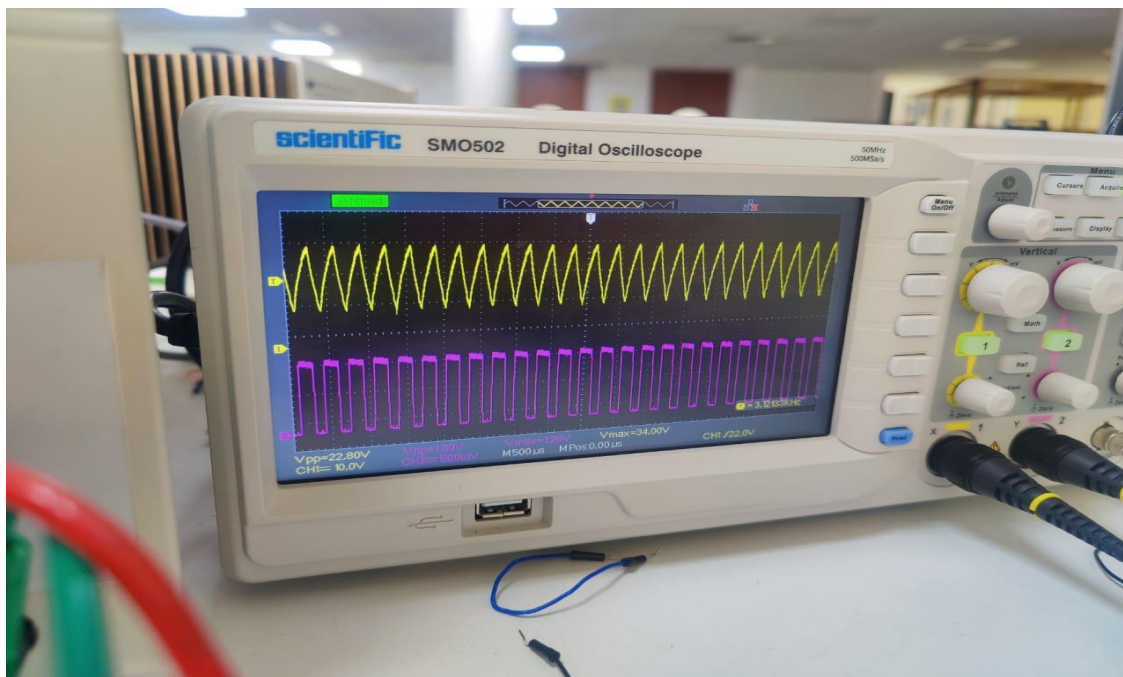


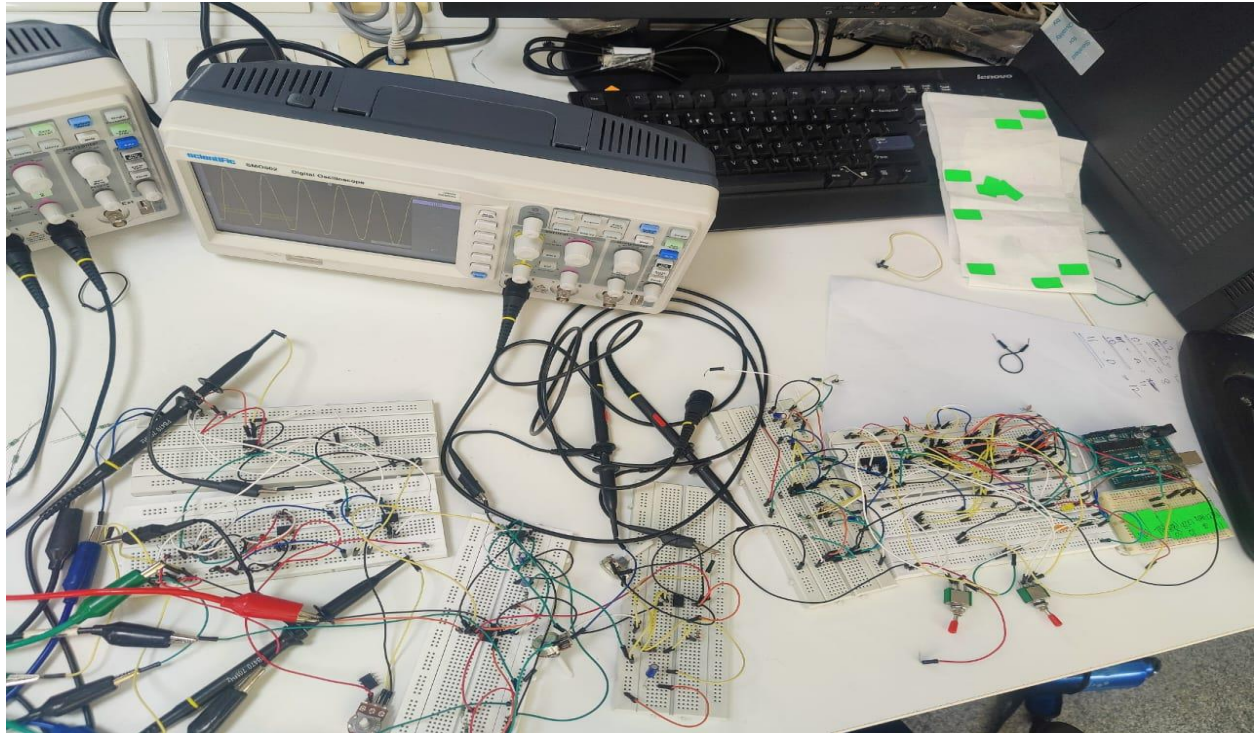


These are the circuits we built :-

Square wave :

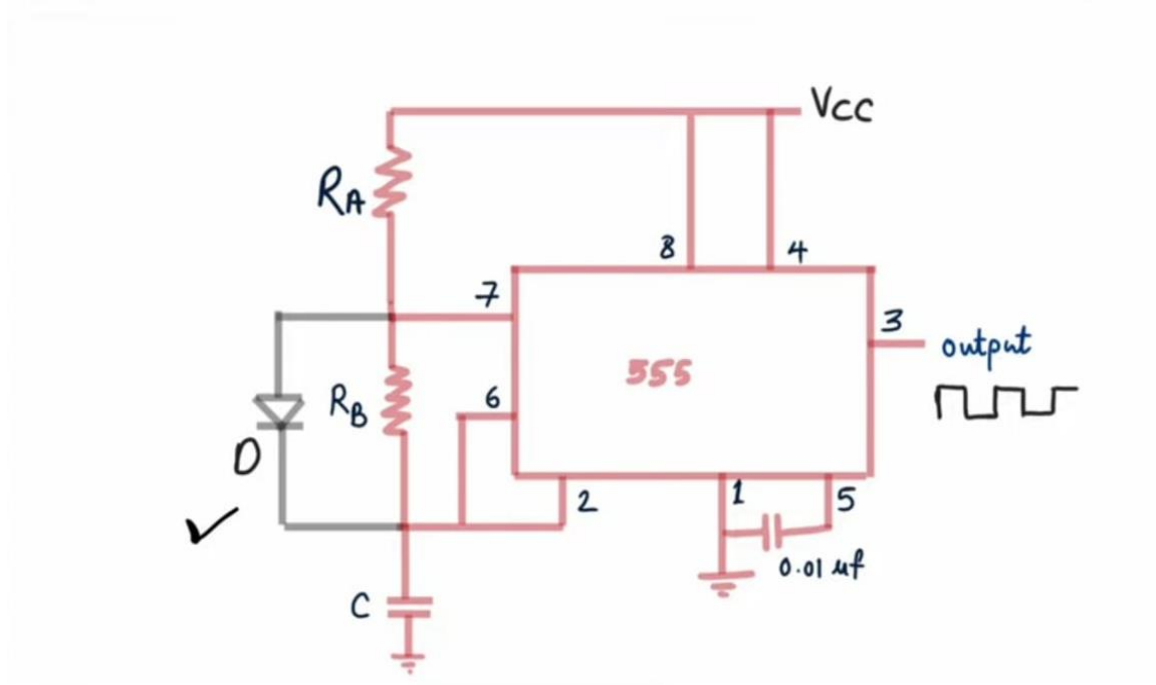


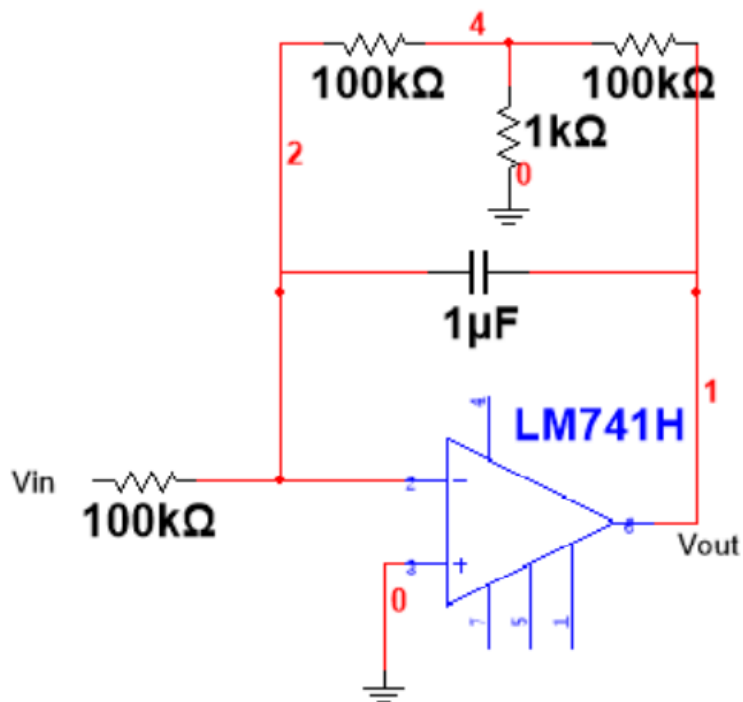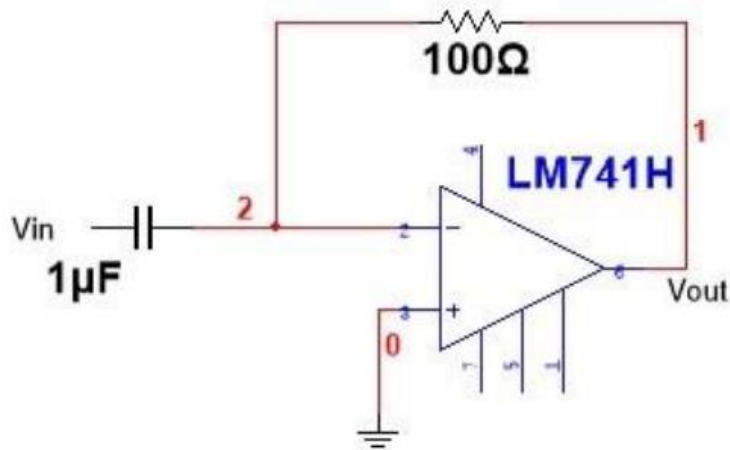Differentiator and Integrator circuits used :




- We integrated square wave to get triangle.
- And we differentiated sine to get cosine wave.

Sine Circuit diagram :

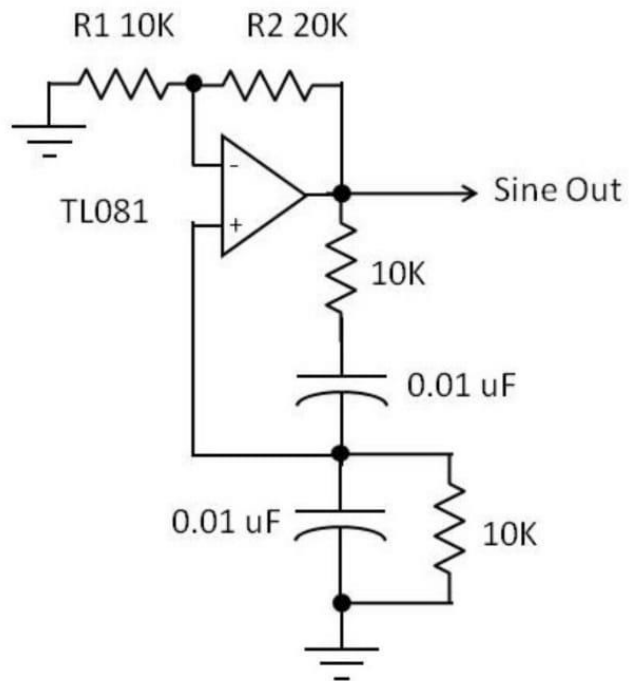

Mux circuit diagram :

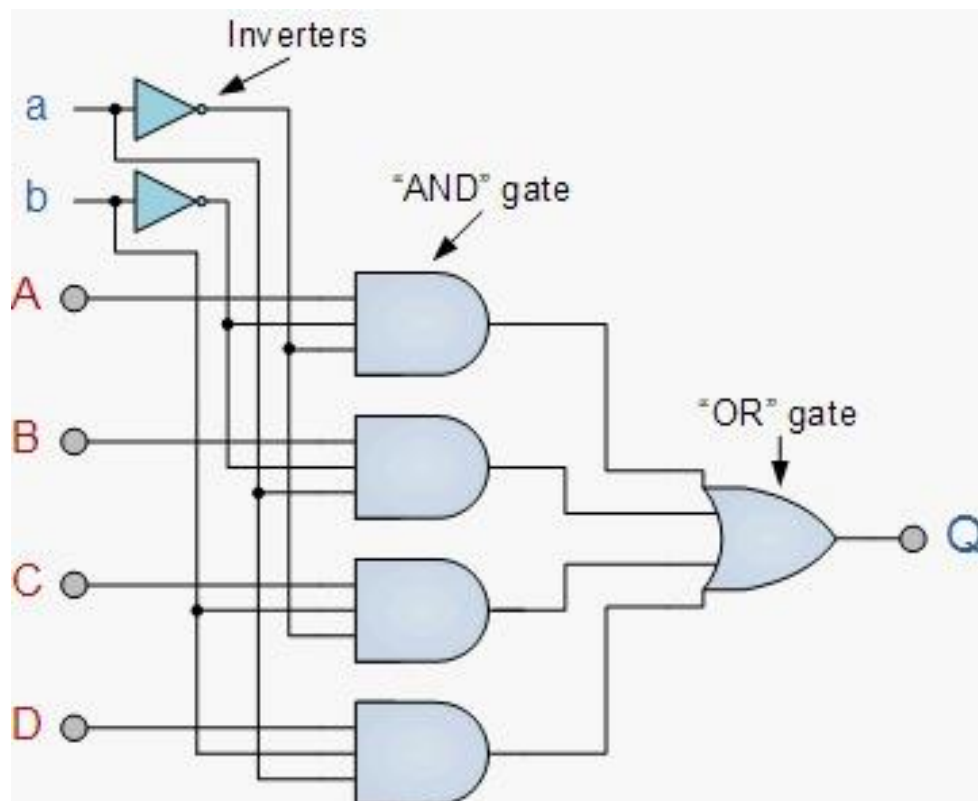

VIDEO LINK :

<https://drive.google.com/drive/folders/1-K3fPfK962oh9QcnRzw2TsVdqeHtAI?usp=sharing>